

Instruction Type	Instruction	Encoding				
		[14:11]	[10:8]	[7:5]	[4:2]	[1:0]
Data Processing	copy	0100	<write reg>	xxx	<read reg>	xx
Data Processing	add	0110	<write reg>	<read reg 1>	<read reg 2>	xx
Data Processing	sub	0111	<write reg>	<read reg 1>	<read reg 2>	xx
Data Processing	neg	0101	<write reg>	xxx	<read reg>	xx
Memory	loadr	0011	<data reg>	xxx	<addr reg>	xx
Memory	storer	0010	xxx	<data reg>	<addr reg>	xx
Immediate	setn	0001	<write reg>	<immediate[7:0]>		
Branch	jumpn	110x	xxx	<immediate[7:0]>		
Branch	jumpr	111x	<addr reg>	xxxxxxxx		
Branch	jeqzn	1000	<data reg>	<immediate[7:0]>		
Branch	jneqzn	1001	<data reg>	<immediate[7:0]>		
Branch	jgtzn	1010	<data reg>	<immediate[7:0]>		
Branch	jltzn	1011	<data reg>	<immediate[7:0]>		
NOP	nop	0000	xxx	xxxxxxxx		

Figure 1: The HMMMM Instruction Set. All register addresses are three bits wide.

The processor exposes the 8-bit address bus, 15-bit data bus, as well as a memory write control signal for the SRAM. The SRAM is assumed to be always enabled, and is assumed to be in read mode when memory write is low.

2.2 Datapath Design

 


Figure 2: Datapath Block Diagram

The chip is split up into two main blocks: the datapath and the controller. The datapath, with a schematic shown in Figure 2, and HDL in Appendix A, handles the processing and routing of data, and includes the register file and the program counter. The datapath layout is a custom block, and it is split into 12 rows. The bottom 8 rows handle the 8-bit data stream, the top 3 rows contain the register file address decoder, and the row in between contains the zipper, where control signals are routed to the datapath from the controller.

 


Figure 3: Proposed Datapath Slice Map

 


Figure 4: Final Datapath Slice Map

The slice map (Figures 3 and 4) outlines the placement of leaf cells and the routing of signals for each of the bottom 8 rows in the datapath. By summing the width of the leaf

cells one can estimate the total size of the datapath (See Figures 7 and 8 for the full chip floorplan).

 


Figure 5: The datapath layout. A version with labelled cells is available in Appendix E.2.

2.3 Controller Design

The controller processes an input instruction to select multiplexer and ALU modes throughout the datapath. The HDL, available in Appendix A, is synthesized into a schematic and layout.

 


Figure 6: The controller layout. A version with labelled cells is available in Appendix E.1.

2.4 Floorplan

The proposed and completed floorplans are given in Figure 7 and Figure 8, respectively. Notable is a $\approx 2\times$ underestimate of datapath width in the proposed floorplan. This was due to a mis-calculation of standard cell width in the project proposal. No major changes to the datapath were made between the proposal and final layout.

This disparity is most clearly seen when examining the slice plans. The proposed and final datapath slice maps have an identical configuration, with the only difference the estimated and final width.

 


Figure 7: Proposed Floorplan

 


Figure 8: Final Floorplan, Units in λ

2.5 Pinout

MOSIS packages the die in a 40 pin DIP. The package pinout in tabular form is provided in Figure 9. Figure 10 provides a graphical view of the device pinout. Pins 19 and 20 are tied to an inverter as a basic manufacturing test.

Pin Number	Pin Function	Pin Direction
1	vdd	power
2	gnd	power
3	vdd	power
4	gnd	power
5	vdd	power
6	gnd	power
7	reset	input
8	clock phase 1	input
9	clock phase 2	input
10-17	address[0:7]	output
18	memwrite	output
19	test_in	input
20	test_out	output
21	gnd	power
22-36	memdata[0:14]	bidirectional
37	vdd	power
38	gnd	power
39	vdd	power
40	gnd	power

Figure 9: The HMMMM pinout. test_in and test_out are the input to and output from an inverter independent from the processor.

 


Figure 10: A graphical view of the HMMMM pinout

3 Verification

The table in Figure 11 summarizes the verification status of HMMMM.

Verification Step	Status
HDL Passing Testbench	Complete
Controller Passing DRC	Complete
Controller Passing LVS	Complete
Controller Passing Testbench	Complete
Datapath Passing DRC	Complete
Datapath Passing LVS	Complete
Datapath Passing Testbench	Complete
Chip Passing DRC	Complete
Chip Passing LVS	Complete
Chip Passing Testbench	Complete
GDS Re-import	Complete
GDS Verification	Complete

Figure 11: HMMMM Verification Status.

3.1 HDL and Schematic Verification

We created a self-checking SystemVerilog testbench and SRAM for controller and datapath verification¹. On simulation initialization, the SRAM loads a 32-instruction program², and initializes address 0x40 to 0x05. This program tests every HMMMM instruction, including less than zero, equal to zero, and greater than zero for all conditional branches.

Successful program execution will lead to the value 0x2D written in address 0x29. If this is not observed (i.e. if the value 0x00 appears in address 0x29), then the processor has malfunctioned. We substituted exported Verilog in for the controller and datapath when designing the controller and datapath schematic, and have ensured that the final design passes the testbench.

3.2 Layout Verification

After finishing each subsection of the chip, we performed LVS (Layout vs Schematic) by extracting the schematic from our layout automatically and then comparing this to our original schematic. This allowed us to test each cell’s final functionality and isolate issues before they became harder to debug later in the design process. We performed this on each schematic level on the chip from leaf cell to the full chip. We finally exported GDS of our

¹The SystemVerilog source is available in Appendix A.1 and A.2

²The testvectors are available in Appendix A.3

chip and ran LVS after re-importing the final fabrication files to ensure that no parts of the chip were broken during the export process.

3.3 Post-Fabrication Test Plan

We aim to produce not just a functional chip, but a full demonstration system implementing a functional chip. This demonstration and testing system will provide:

- Software-defined SRAM and processor clocks through a Lattice FPGA with onboard non-volatile configuration memory. This allows for non-volatile program storage.
- All HMMMM I/O accessible from 0.1” headers and tri-state buffers
- A digitally-controlled variable-voltage processor power supply, implemented through an LM317 and digital potentiometer
- A shunt resistor to measure HMMMM current requirements, and an associated ADC
- Low-voltage level shifters for all processor interfaces
- LED arrays for address and data bus visualization
- A switch bank for hand-programming the SRAM

Initial testing will involve loading the HMMMM program described in Section 3.1 onto the FPGA SRAM, and testing whether the physical chip correctly executes the program. If this test is successful, we will investigate the IV characteristics of the processor, including transistor response to low voltages. If this test fails, we will follow the following debugging process:

1. Check resistance between vdd and gnd. A short here indicates a completely nonfunctional chip. If this occurs, we will try re-testing with another chip
2. Check inverter behavior across test pins 19 and 20. This is a simple test of the fabrication process, and a failure here indicates a larger problem with our layout. If this occurs, we will try re-testing with another chip
3. Debugging steps past the above points are contingent on the observed symptoms

Finally, we will implement simple assembly programs seen in CSCI005 and CSCI042 to use the device as a demonstration tool.

4 Logistics

4.1 Design Time

The design time breakdown is illustrated in Figure 12.

Design Component	Design Time (Hours)	Verification Time (Hours)
Testbench HDL	2	1
SRAM HDL	1.5	0.5
Datapath HDL	10	2
Datapath Schematic	6	1.5
Datapath Layout	9	4
Controller HDL	4	3
Controller Schematic	7	2
Controller Layout	2	1
Chip Schematic	3	4
Chip Layout	2	1
Chip Export	1	0.5
Leaf Cell	1	0.5

Figure 12: Design time breakdown for the HMMMM processor

4.2 File Locations

All human-readable source files are included in the appendix to this report. Design and testbench HDL, testvectors, GDS³, and PDF⁴. of this report are available on the project GitHub⁵.

Cadence design files are accessible in the repository under directory `cadence_design_files`. Design components are available under the following libraries and cells described in Figure 13.

³https://github.com/VLSIPProject2019/vlsi-2019/exported_chip.gds

⁴https://github.com/VLSIPProject2019/vlsi-2019/final_report.pdf

⁵<https://github.com/VLSIPProject2019/vlsi-2019>

Design Component	Library	Cell
Full Chip	HMMM	chip
Chip (no padframe)	HMMM	top
Padframe	HMMM	padframe
Datapath	HMMM	datapath
Controller	HMMM_Synth	controller

Figure 13: Cadence design file locations

5 References

“Documentation for Hmmm (Harvey Mudd Miniature Machine)” *Harvey Mudd College*, Fall, 2018. Web.

Appendix

A HDL Source Code

```

// Microprocessor for E190AT: VLSI Design Project
// Authors: Erik Meike, Caleb Norfleet, & Kaveh Pezeshki
// Created Spring 2019

module top (input logic ph1, ph2, reset,
            output logic MemWrite,
            output logic [7:0] Adr,
            input logic [14:8] MemData1,
            inout logic [7:0] MemData2);

logic PCEnable, AdrSrc, RA1Src, InstrSrc, RegWrite;
logic TwoRegs, ALUSub, negative, zero, RegWLoadSrc;
logic [1:0] PCSrc, RegWriteSrc;
logic [7:0] WriteData;
logic [14:8] instr1;

// tristate for handling write data
assign MemData2[7:0] = (MemWrite ? WriteData : 8'bzz);

controller c(ph1, ph2, reset, negative, zero, RegWLoadSrc,
             RA1Src, PCEnable, AdrSrc, InstrSrc, RegWrite,
             TwoRegs, ALUSub, PCSrc, RegWriteSrc, MemWrite,
             MemData1, instr1);

// datapath dp(Adr, negative, zero, MemData2[7:0], ALUSub,
//           AdrSrc, instr1[10:8], InstrSrc, MemWrite,
//           PCEnable, PCSrc, RA1Src, RegWLoadSrc, RegWrite,
//           RegWriteSrc, TwoRegs, ph1, ph2, reset );

datapath dp(ph1, ph2, reset, PCEnable, AdrSrc, InstrSrc,
            RA1Src, RegWrite, MemWrite, TwoRegs, ALUSub,
            RegWLoadSrc,
            PCSrc, RegWriteSrc, instr1[10:8], MemData2, WriteData,
            Adr, negative, zero);

endmodule

module datapath (input logic ph1, ph2, reset,
                  input logic PCEnable, AdrSrc, InstrSrc, RA1Src,
                  RegWrite,
                  input logic MemWrite, TwoRegs, ALUSub,
                  RegWLoadSrc,
                  input logic [1:0] PCSrc, RegWriteSrc,
                  input logic [10:8] instr1,

```

```

    input logic [7:0] MemData2,
    output logic [7:0] WriteData,
    output logic [7:0] Adr,
    output logic negative, zero);

logic[7:0] PC, PCNext, PCPlus1;
logic[7:0] Result, SrcA, SrcB, Imm, WD3;
logic[7:0] WD3Temp, WD3Temp2, RD1, RD2;
logic[2:0] RA1, RA2, WA3;
logic[7:0] instrTemp2, instr2;

// next PC logic
adder #(8) pcAdd(PC, 8'b1, 1'b0, PCPlus1);
fopenr #(8) pcReg(ph1, ph2, reset, PCEnable, PCNext, PC);
mux3 #(8) pcMux(PCPlus1, Imm, RD1, PCSrc, PCNext);

// data memory
mux2 #(8) adrMux(PC, RD2, AdrSrc, Adr);
assign WriteData = RD1;

// instruction handling
flopr #(8) instrReg2(ph1, ph2, reset, MemData2, instrTemp2);
mux2 #(8) instrMux2(instrTemp2, MemData2, InstrSrc, instr2);

// register read/write logic
mux3 #(8) wd3Mux(Imm, MemData2[7:0], Result, RegWriteSrc, WD3Temp);
flop #(8) wd3Reg(ph1, ph2, reset, WD3Temp, WD3Temp2);
mux2 #(8) loadMux(WD3Temp2, WD3Temp, RegWLoadSrc, WD3);
regfile rf(ph1, ph2, reset, RegWrite, RA1, RA2, WA3, WD3, RD1, RD2);
mux2 #(3) ra1Mux(instr2[7:5], instr1[10:8], RA1Src, RA1);
assign RA2 = instr2[4:2];
assign WA3 = instr1[10:8];
assign Imm = instr2[7:0];

// zero and negative for conditional branching
assign negative = RD1[7];
assign zero = ~(RD1);

// ALU logic
assign SrcB = {8{ALUSub}} ^ RD2;
// ^same as: mux2 #(8) srcBMux(RD2, notRD2, ALUSub, SrcB);
assign SrcA = {8{TwoRegs}} & RD1;
// ^same as: mux2 #(8) srcAMux(8'b0, RD1, TwoRegs, SrcA);

```

```

    adder #(8) alu(SrcA, SrcB, ALUSub, Result);
endmodule/*/


module controller (input logic ph1, ph2, reset,
                    input logic negative, zero,
                    output logic RegWLoadSrc, RA1Src,
PCEnable, AdrSrc,
                    output logic InstrSrc, RegWrite, TwoRegs,
ALUSub,
                    output logic[1:0] PCSrc, RegWriteSrc,
                    output logic MemWrite,
                    input logic[14:8] MemData1,
                    output logic[14:8] instr1);

logic state, stateBar, condBranch;
logic branch, unconditional, regJumpLoc;
logic[3:0] funct;
logic[14:8] instrTemp1;

// instruction handling
flopr #(7) instrReg1(ph1, ph2, reset, MemData1, instrTemp1);
mux2 #(7) instrMux1(instrTemp1, MemData1, InstrSrc, instr1);
assign funct = instr1[14:11];

// cycle clock "FSM" (0=instr read, 1=load/write back)
// note: branch instructions only require one cycle
flopr #(1) stateReg(ph1, ph2, reset, stateBar & ~branch, state);
assign stateBar = ~state;

assign PCEnable = state | branch;
assign AdrSrc = state;
assign InstrSrc = ~reset & stateBar;

// branch
assign branch = funct[3];
assign unconditional = funct[2];
assign regJumpLoc = funct[1];
condcheck cc(funct[1:0], negative, zero, condBranch);
assign PCSrc = (branch & (unconditional | condBranch)) ?
                ((unconditional & regJumpLoc) ?
                 2'b10 : 2'b01) : 2'b00;
assign RA1Src = branch;

// data processing

```

```

assign TwoRegs = funct[1];
assign ALUSub = funct[0];

// writeback
assign MemWrite = (state & (funct == 4'b0010)) & ~reset;
// ^Note: added &~reset so that first instruction can be loaded at init
assign RegWrite = state & ~branch & (funct[2] | funct[0]);
always_comb
    if(funct[2])
        RegWriteSrc = 2'b10; // Result
    else if(funct[1])
        RegWriteSrc = 2'b01; // ReadData
    else
        RegWriteSrc = 2'b00; // Imm
assign RegWLoadSrc = (funct == 4'b0011);
endmodule

```

```

module condcheck (input logic[1:0] branchType,
                  input logic negative, zero,
                  output logic condBranch);

always_comb
    case(branchType) // branchType = {isZero, greaterThan}
        2'b00: // jeqzn
            condBranch = zero;
        2'b01: // jneqzn
            condBranch = ~zero;
        2'b10: // jgtzn
            condBranch = ~negative & ~zero;
        2'b11: // jltn
            condBranch = negative; // if negative then also nonzero
    default:
        condBranch = 1'bx;
    endcase
endmodule

```

```

module adder #(parameter WIDTH=8)
    (input logic [WIDTH-1:0] a, b,
     input logic cin,
     output logic [WIDTH-1:0] y);

    assign y = a + b + cin;
endmodule

```

// note: regfile copied from MIPS8 design

```

module regfile #(parameter WIDTH = 8)
    (input logic ph1, ph2, reset,
     input logic we3,
     input logic [2:0] ra1, ra2, wa3,
     input logic [WIDTH-1:0] wd3,
     output logic [WIDTH-1:0] rd1, rd2);

    // note: can't read PC in HMMM
    // three ported register file
    // read two ports combinatorially
    // write third port during phase2 (second half-cycle)

    logic [WIDTH-1:0] RAM [7:0];

    always_latch
        if (ph2 & we3) RAM[wa3] <= wd3;

        assign rd1 = RAM[ra1];
        assign rd2 = RAM[ra2];
endmodule/*/


module mux2 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1,
     input logic s,
     output logic [WIDTH-1:0] y);
    assign y = s ? d1 : d0;
endmodule

module mux3 #(parameter WIDTH = 8)
    (input logic [WIDTH-1:0] d0, d1, d2,
     input logic [1:0] s,
     output logic [WIDTH-1:0] y);
    // note: 11 is treated as the same as 10
    assign y = s[1] ? (d2) : (s[0] ? d1 : d0);
    // alternative:
    // assign y = s[1] ? (s[0] ? 8'bx : d2) : (s[0] ? d1 : d0);
endmodule

module flop #(parameter WIDTH = 8)
    (input logic ph1, ph2, reset,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);
    logic[WIDTH-1:0] nextQ;

```

```

always_latch
    if (ph1) q <= nextQ;
always_latch
    if (ph2) nextQ <= d;
endmodule

// taken from MIPS8
module flop #(parameter WIDTH = 8)
    (input logic ph1, ph2, reset,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);
    logic[WIDTH-1:0] nextQ;
    always_latch begin
        if (ph1)
            q <= nextQ;
    end
    always_latch begin
        if (ph2)
            if (reset) nextQ <= 0;
            else      nextQ <= d;
    end
endmodule

// taken from MIPS8
module fopenr #(parameter WIDTH = 8)
    (input logic ph1, ph2, reset, en,
     input logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);
    logic [WIDTH-1:0] d2, resetval;
    assign resetval = 0;

    mux3 #(WIDTH) enrmux(q, d, resetval, {reset, en}, d2);
    flop #(WIDTH) f(ph1, ph2, reset, d2, q);
endmodule

```

B HDL Testbench Code

B.1 Testbench

```
// Microprocessor Testbench for E190AT: VLSI Design Project
// Authors: Erik Meike, Dominique Mena, Caleb Norfleet, & Kaveh Pezeshki
// Created Spring 2019
```

```
// Set delay unit to 1 ns and simulation precision to 0.1 ns (100 ps)
`timescale 1ns / 100ps
```

```
module testbench();
```

```
    // Processor signals
```

```
    logic clk1, clk2;
    logic reset;
```

```
    // Memory interface
```

```
    logic MemWrite; // active high
    wire [15:0] MemData;
    logic [7:0] Adr;
```

```
    // Internal Signals and Combinational Logic
```

```
    // To be handled on PCB
```

```
    // SRAM interface
```

```
    logic ce; // chip enable, active low
    logic oe; // output enable, active low
    logic we; // write enable, active low
```

```
    assign ce = 1'b0;
```

```
    assign oe = MemWrite; // output enabled when not writing
    assign we = !MemWrite;
```

```
    // Instantiating the processor
```

```
top dut(clk1, clk2, reset, MemWrite, Adr, MemData[14:8], MemData[7:0]);
```

```
    // Instantiating the SRAM
```

```
    sram mem(ce, oe, we, Adr, MemData);
```

```
    // Opening the testvector file and setting up memory
```

```
    // Pulsing reset to initialize the processor
```

```
initial
```

```
begin
```

```
    // NOTE: sram module automatically initializes memory
```

```

// from memfile.dat
clk2 = 0; reset = 1; #19; reset = 0;
end

// Creating the clock
always
begin
    clk1 <= 1; # 3; clk1 <= 0; # 2;
    clk2 <= 1; # 3; clk2 <= 0; # 2;
end

// Executing Instructions
always @(negedge clk2)
begin
    if(MemWrite) begin
        if(MemData === 16'bzzzzzzz00101101) // && dut.dp.PC === 8'd32
            $display("Test Successful!");
        else
            $display("Test Failed with MemData = %b", MemData);
            //$display("Test Failed on Line %d with MemData = %b",
dut.dp.PC, MemData);
            $stop;
    end
end
endmodule

```

B.2 SRAM

```

// Generic SRAM for E190AT: VLSI Design Project
// Authors: Erik Meike, Dominique Mena, Caleb Norfleet, & Kaveh Pezeshki
// Created Spring 2019

module sram #(parameter ADDR_WIDTH=8,
               parameter DATA_WIDTH=16)
(
    input logic ce, // Active low chip enable
    input logic oe, // Active low output enable
    input logic we, // Active low write enable

    input logic [ADDR_WIDTH-1:0] adr, // Address bus
    inout wire [DATA_WIDTH-1:0] data // Data bus
);

// internal variables
reg [DATA_WIDTH-1:0] data_out; // caching requested data
reg [DATA_WIDTH-1:0] mem [((ADDR_WIDTH**2)-1:0)]; // memory

// Combinational logic: memory read tri-state
assign data = (!ce && we && !oe) ? data_out : {((DATA_WIDTH){1'b0})};

// Memory Read / Write Latches
always_latch
    if (!ce && !we && oe) // if writing data
        mem[adr] = data;
    else if (!ce && we && !oe) //if reading data
        data_out = mem[adr];

// Initial block to set up memory for testing
initial begin
    $readmemb("memfile.dat", mem);
end
endmodule

```

B.3 Testvectors

	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P
1	Program Memory															
2	Assuming base 10															
3	addr	Instruction	R0	R1	R2	R3	R4	R5	R6	R7			Notes	Mem		
4	0	setn R0, 40	40	x	x	x	x	x	x	x						
5	1	loadr R1, R0	40	5	x	x	x	x	x	x						5 already in addr 64
6	2	copy R2, R1	40	5	5	x	x	x	x	x						
7	3	neg R2, R2	40	5	-5	x	x	x	x	x						
8	4	add R3, R0, R2	40	5	-5	35	x	x	x	x						
9	5	sub R4, R0, R2	40	5	-5	35	45	x	x	x						
10	6	jumpn 8	40	5	-5	35	45	x	x	x			sets R4 incorrectly if jump fails			
11	7	setn R4, 0	40	5	-5	35	0	x	x	x			We want R4 to remain 64 to pass test			
12	8	setn R5, 11	40	5	-5	35	45	11	x	x						
13	9	jmpnr R5	40	5	-5	35	45	11	x	x			sets R4 incorrectly if jump fails			
14	10	setn R4, 0	40	5	-5	35	0	11	x	x						
15	11	setn R6, 0	40	5	-5	35	45	11	0	x						
16	12	jeqzn R6, 14	40	5	-5	35	45	11	0	x			should jump			
17	13	setn R4, 0	40	5	-5	35	0	11	0	x						
18	14	jeqzn R1, 30	40	5	-5	35	45	11	0	x			should not jump			
19	15	jeqzn R2, 30	40	5	-5	35	45	11	0	x			should not jump			
20	16	jnezn R1, 18	40	5	-5	35	45	11	0	x			should jump			
21	17	setn R4, 0	40	5	-5	35	0	11	0	x						
22	18	jnezn R2, 20	40	5	-5	35	45	11	0	x			should jump			
23	19	setn R4, 0	40	5	-5	35	0	11	0	x						
24	20	jnezn R6, 30	40	5	-5	35	45	11	0	x			should not jump			
25	21	jgtzn R1, 23	40	5	-5	35	45	11	0	x			should jump			
26	22	setn R4, 0	40	5	-5	35	0	11	0	x						
27	23	jgtzn R2, 30	40	5	-5	35	45	11	0	x			should not jump			
28	24	jgtzn R6, 30	40	5	-5	35	45	11	0	x			should not jump			
29	25	jltzn R2, 27	40	5	-5	35	45	11	0	x			should jump			
30	26	setn R4, 0	40	5	-5	35	0	11	0	x						
31	27	jltzn R1, 30	40	5	-5	35	45	11	0	x			should not jump			
32	28	jltzn R6, 30	40	5	-5	35	45	11	0	x			should not jump			
33	29	jumpn 31	40	5	-5	35	45	11	0	x						
34	30	setn R4, 0	40	5	-5	35	45	11	0	x			Fails test			
35	31	setn R7, 41	40	5	-5	35	45	11	0	41						
36	32	storer R4, R7	40	5	-5	35	45	11	0	41			Test succeeds if 45 written in addr 65			
37	Data Memory															
38	Addr	Stored Val														
39	40	5											set before test			
40	41	45, 0											45 if test passes, 0 if test fails			
41																

Figure 14: The HMMMM Test Program, with annotated register states after each instruction

C Custom Leaf Cell: Tri-State Buffer

C.1 Schematic

 


Figure 15: Schematic for the custom tri-state buffer leaf cell

C.2 Symbol

 


Figure 16: Symbol for the custom tri-state buffer leaf cell

C.3 Layout

 


Figure 17: Layout for the custom tri-state buffer leaf cell

D Layouts

D.1 Controller

 


Figure 18: Layout image of the Hmmm Controller. Each named block denotes a sub-cell

D.2 Datapath

 


Figure 19: Layout image of the HMMM datapath. Each named block denotes a sub-cell